



How many **unique** ways can you find to break the circuit?

*Break **one thing**...*

*Then **fix it**...*

Then break something else!

Can you add a **second LED** to the circuit?

<https://www.tinkercad.com/things/csMdgkbPIYr>